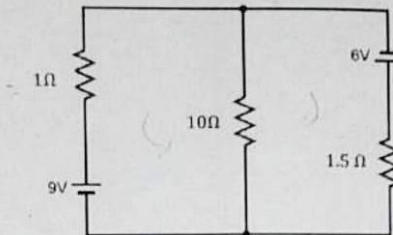


Marks: 52%


Time: 3 Hours

**Section-A**


1. a) Show that in any electrical network the incoming current is equal to outgoing current. 3  
 b) From the circuit shown below determine the current through 10 Ohm resistor using i) Thevenin's theorem and ii) Norton's theorem. 5%



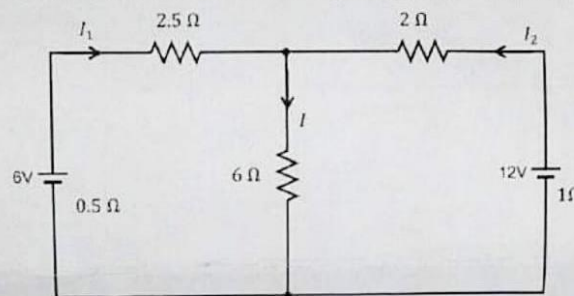
- 2.a) Determine the number of branches and nodes in the figure given below. Find out the current  $I_1$  and  $I_2$ . 2



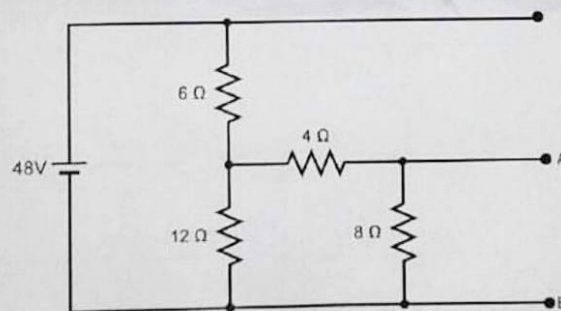- b) Define Thevenin's voltage and Thevenin's resistance with an example. 3  
 c) Calculate the value of  $V_{TH}$  and  $R_{TH}$  between terminal A and B of the following figure: 3%



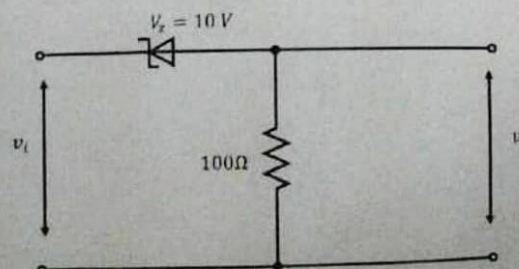
3. a) Why Si or Ge is not used to fabricate LEDs? 2%  
 b) What is LCD? Why does it require extremely low power to operate LCDs? 3  
 c) Why P-N photodiode is known as one of the fastest photo-detector? What are the other uses of P-N photodiode except photo-detector? 3  
 4. a) What is a Zener diode? 1  
 b) Show the V-I characteristics of a Zener diode. 2%  
 c) Calculate the value of  $v_o$  for the given circuit for i)  $v_i = 5V$  ii)  $v_i = 10V$  and iii)  $v_i = 15V$






## Section-B

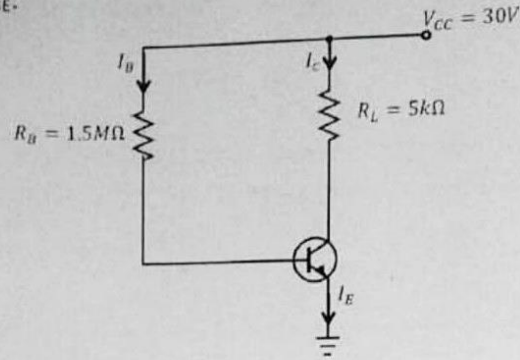
- 5.a) What will happen if a transistor is not biased properly?  
 b) For the amplifier drawn below i) draw the load line and ii) mark the Q point.  
 Assume  $\beta=100$  and neglect  $V_{BE}$ .



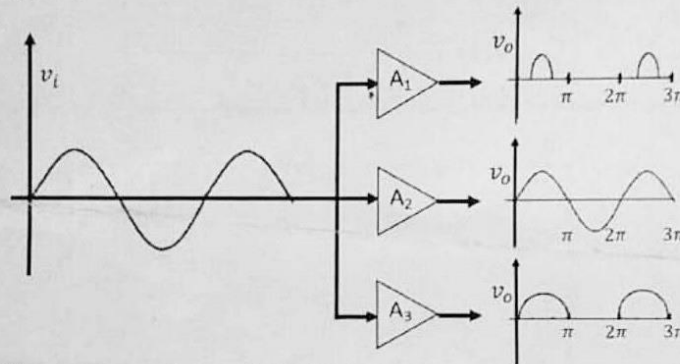
- c) The inputs and outputs of three amplifiers  $A_1$ ,  $A_2$  and  $A_3$  are shown below. Classify the amplifiers depending on their outputs. 1 3/4



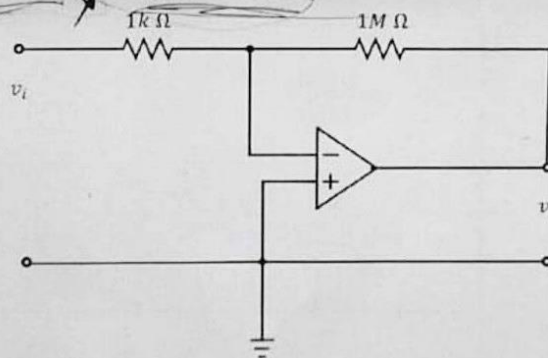- 6.a) What is an OP-AMP? What are the uses of OP-AMP?  
 b) Discuss the basic characteristics of an ideal OP-AMP.  
 c) For the following amplifier (assume the OP-AMP is ideal) determine the following -  
 i) voltage gain ii) input resistance iii) output resistance



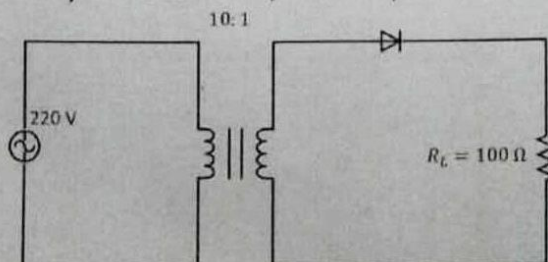- 7.a) What is an oscillator?  
 b) Discuss the conditions for oscillation.  
 c) Design a Hartley oscillator which has to be tunable over 500 kHz to 1000 kHz. The values of the two inductors are  $50 \mu H$  each. Neglect the effect of mutual inductance.  
 8.a) What do you mean by Zener breakdown and avalanche breakdown?  
 b) Draw the circuit diagram of a full-wave bridge rectifier.  
 c) Consider  $R_L$  is the load resistance in the half-wave rectifier shown below, determine i) rms value of load voltage ii) power absorbed by the load and iii) efficiency of the rectifier.



$$A_v = \frac{R_E}{R_L}$$