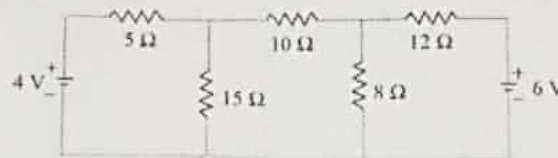


University of Rajshahi  
Department of Computer Science and Engineering  
B.Sc. Engineering Part-I Odd Semester Examination 2020  
Course: EEE-1131 (Electrical Circuits and Electronics) (2018-2019)  
Course: APPE-1131 (Electrical Circuits and Electronics) (2017-2018)  
Time: 03 Hours Full Marks: 52.5


[N.B. Answer 06 (Six) questions taking any 03 (Three) questions from each section.  
The figures in the right margin indicate full marks.]

Section-A

- ✓ (a) Why domestic appliances are connected in parallel? Give comparison with series circuit. 3
- ✓ (b) State and explain Kirchhoff's voltage law. 2
- (c) A network is arranged as shown in the following figure. Determine the value of currents in each resistor. 3.75



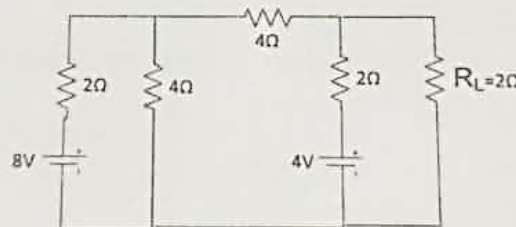- 2✓ (a) State and explain superposition theorem. 4.75
- (b) Using Thevenin's theorem, find the current through the  $R_L = 2\Omega$  as in the following figure: 4




$V = IR_L$   
 $I = \frac{V}{R_L}$

3. (a) What is a rectifier? Show the circuit diagram of a full wave rectifier.
- (b) Define voltage regulation (VR) and Peak Inverse Voltage (PIV).
- (c) A half wave rectifier using Ge diode has secondary emf of  $20 V_{p-p}$ . Diode forward resistance is  $0.25 \Omega$  and load resistance is  $1000 \Omega$ . Find i) Maximum load voltage ii) DC load voltage and iii) efficiency. 2.7
4. (a) Why transistor biasing is necessary? Discuss any one method used for transistor biasing.
- (b) For a certain transistor,  $I_c = 5.505 \text{ mA}$ ,  $I_B = 50 \mu\text{A}$ ,  $I_{co} = 5 \mu\text{A}$ . Determine  
i) The value of  $\alpha$ ,  $\beta$  and  $I_E$ .  
ii) The new level of  $I_B$  required to make  $I_c = 10 \text{ mA}$ .
- (c) Show the relationship between  $\alpha$  and  $\beta$  for a transistor.

$R_{th} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$

### Section-B

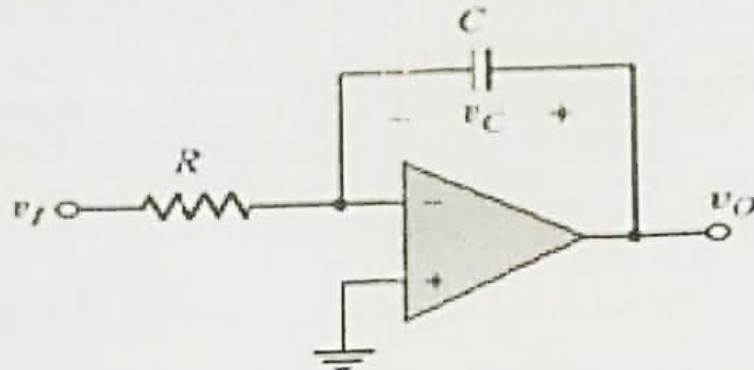5. (a) What is an OP-AMP? What are the basic characteristics of an ideal OP-AMP? 3  
 (b) What do you mean by virtual ground of an OP-AMP? Explain. 1.75  
 (c) A 10mV, 5KHz sinusoidal signal is applied to the input of an OP-AMP integrator as shown below for which  $R = 50K$  and  $C = 2\mu F$ . Find the output voltage. 4



6. (a) How is an oscillator different from an amplifier? Mention some of the applications of an oscillator. 4.75  
 (b) Design a Hartley oscillator which has to be tunable over 500 kHz to 1000 kHz. The values of the two inductors are 50  $\mu H$  each. Neglect the effect of mutual inductance. 4

7. (a) What is LCD? Describe the working principle of LCD. 3.75  
 (b) What are the advantages of LCD? 2  
 (c) What is P-N photodiode? Why it works in reverse biased condition? 3

8. (a) What is a Zener diode? 1  
 (b) Explain the V-I characteristics of a Zener diode. 3  
 (c) Show that Zener diode can be used as voltage regulator. 4.75

