

2013:

2.(b) Here,

$$I_1 = \frac{V_1}{r_1} = \frac{6}{0.5} = 12 \text{ Amp.}$$

$$I_2 = \frac{V_2}{r_2} = \frac{12}{1} = 12 \text{ Amp.}$$


Here, let current through 6Ω is

$$I_3 = I_1 + I_2 = 24 \text{ Amp}$$

$$V = IR = I_3 \times 6 = 24 \times 6 = 144 \text{ V}$$

~~Sir, I think the above math is wrong. Sir~~
~~please check.~~

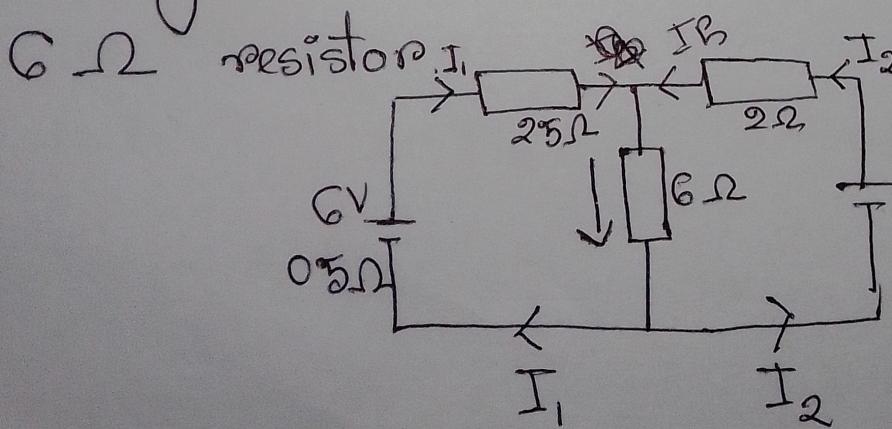2(b) In figure-1, let the battery e.m.f's be 6V & 12V
their internal resistance 0.5Ω & 1Ω . The values
of resistances are as indicated. Find the current
flowing in different branches & voltage across



$$I_1 = I_2 + I_p + I_3$$

1. (a) For a certain transistor, $I_C = 5.505 \text{ mA}$, $I_B = 50 \mu\text{A}$
 $I_{CO} = 5 \mu\text{A}$.

Determine i) value of α , β & I_E .
ii) the new level of I_B required to make $I_C = 10 \text{ mA}$.

$$i) \beta = \frac{I_C}{I_B} = \frac{5.505 \times 10^{-3}}{50 \times 10^{-6}} = 110.1$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{110.1}{1 + 110.1} = 0.990$$

$$I_B = I_B + I_C = (50 \times 10^{-6} + 5.505 \times 10^{-3}) \text{ A} \\ = 5.55 \times 10^{-3} \text{ A} \\ = 5.55 \text{ mA}$$

$$ii) \beta = \frac{I_C}{I_B} \quad I_C = 10 \text{ mA}$$

$$I'_B = \frac{I_C}{\beta} = \frac{10 \times 10^{-3}}{110.1} = 90 \times 10^{-6} = 90 \mu\text{A}$$

$$= \frac{5.505 \times 10^{-3}}{110.1}$$

New, $I'_B = 90 \mu\text{A}$

$$e^{5 \times 10^{-5}}$$

$$\text{old } I_B = 50 \mu\text{A}$$

$\therefore \Delta \text{ Increase} = 40 \mu\text{A}$


$$q = A \cdot R \cdot I^2 = \frac{0.01}{8.8} = \frac{V}{R} = I$$

2014

1. (b) Calculate i) equivalent resistances across the terminal of supply.

ii) total current supplied by the source.

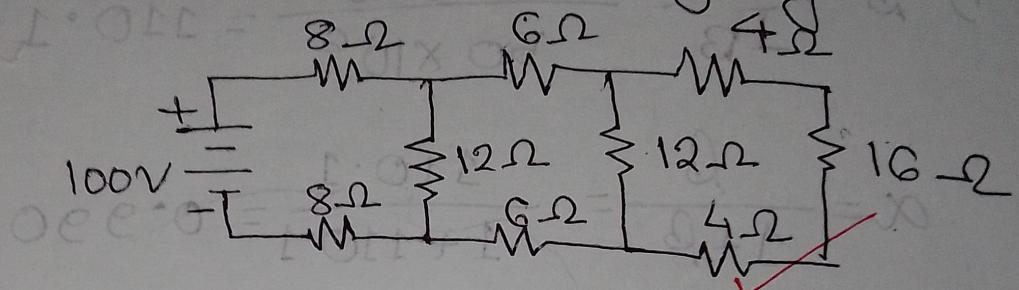(iii) Power delivered to 16Ω resistor as shown in following fig-1.




$$\begin{aligned}
 \text{i)} R_f &= 8 + ((6 + ((4+16+4) \parallel 12) + 6) \parallel 12) + 8 \\
 &= 8 + 16 + ((6 + (24 \parallel 12) + 6) \parallel 12) \\
 &= 16 + ((12 + \frac{24 \times 12}{24+12}) \parallel 12) \\
 &= 16 + ((12 + 8) \parallel 12) \\
 &= 16 + 20 \parallel 12 \\
 &= 16 + \frac{20 \times 12}{20+12} \\
 &= 16 + 7.5 \\
 &= 23.5 \Omega
 \end{aligned}$$

∴ $I = \frac{V}{R} = \frac{100}{23.5} = 4.255 \text{ Amp.}$

$$\text{iii) } I_1 = 4.25 \text{ Amp.}$$

$$I_2 = \frac{12}{12+20} \times I_1 = 1.593 \text{ Amp.}$$
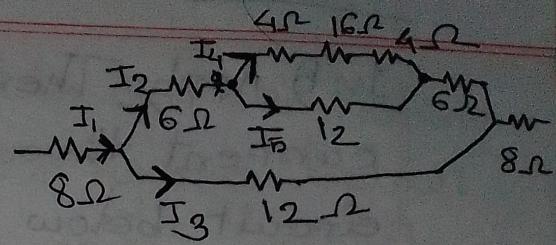
$$I_4 = \frac{12}{12+24} \times I_2 = 0.531 \text{ Amp.}$$



$$\therefore P \text{ through } 16\Omega, P = I^2 R = (0.531)^2 \times 16 \\ = 4.511 \text{ W}$$


~~Ques~~ Sir, please differentiate between avalanche & zener breakdown. It contains 3 mark. I am unable to find suitable differences.

Avalanche breakdown: occurs when the ionisation of electron & hole recombination occurs.

2016

1. B) Apply Thevenin's theorem to calculate the current through the 5Ω resistor of the circuit below :

Solⁿ:

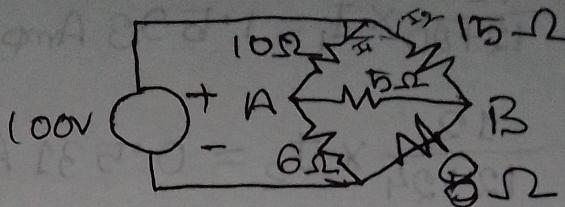

Removing load resistance,

$$I_1 = \frac{V}{15+8} = \frac{100}{23} = 4.347 \text{ A}$$

$$I_2 = \frac{V}{10+6} = \frac{100}{16} = 6.25 \text{ A}$$

Voltage at point B & A,

$$V_B = 100 - 15 \times I_1 = 34.75 \text{ V}$$

$$V_A = 100 - 10 \times I_2 = 37.5 \text{ V.}$$

$$V_{th} = V_A - V_B = 2.75 \text{ V.}$$


~~$$R_{th} = \frac{16 \times 23}{16 + 23} = 9.44 \Omega$$~~

$$I_{th} = \frac{V_{th}}{R_{th}} = \frac{2.75}{9.44} = 0.291 \text{ A.}$$

$$I_L = \frac{R_{th}}{R_L + R_{th}} \times I_{th} = \frac{9.44}{9.44 + 5} \times 0.291 \\ = 0.190 \text{ A (Ans)}$$

2c) Apply Norton's theorem to calculate current flowing through the terminal AB of the figure below:

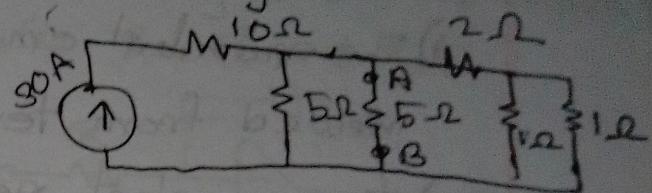
Solⁿ: While determining equivalent resistance the load resistance is open.



$$\begin{aligned}
 R_N &= 10 + \left((2 + (1 \parallel 1)) \parallel 5 \right) \\
 &= 10 + \left(2 + \frac{1 \times 1}{1+1} \right) \parallel 5 \\
 &= 10 + \frac{2 \cdot 5 \times 5}{2 \cdot 5 + 5} = 11.67 \Omega
 \end{aligned}$$

$$V = IR_N = 30 \times 11.67 = 350.1 \text{ V}$$
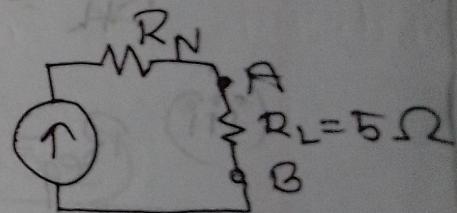
$$I_{AB} = \frac{V_N}{R_L} = \frac{350.1}{5} = 70.02 \text{ A} \quad (\text{Ans})$$



2016
6. (c) → Optoisistor very complex math. Did not write the question

$$1-x \geq 0$$

$$-x \geq -1$$

$$x \leq 1$$

2017.

3. b) With reference to the network of fig-2 by applying Thvenin's theorem find:


i) The equivalent emf of the network when viewed from terminal A & B.

ii) The equivalent resistance of the network when looked from terminal AB.

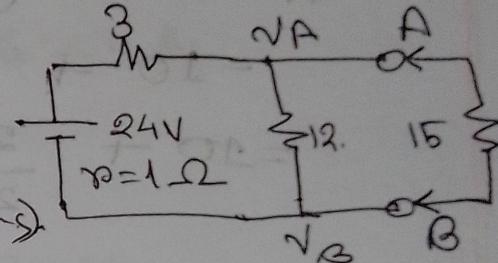iii) Current in the load resistance R_L of 15Ω

Ans Solⁿ:

$$\text{i)} V_{Th} = \frac{12}{3+12} \times 24 = 19.2 \text{ V.} \quad (\text{Ans})$$



$$\text{ii)} R_{Th} = \frac{3 \times 12}{3+12} = 2.4 \Omega \quad (\text{Ans}),$$

$$\text{(iii)} R_{eq} = 3 + \frac{15 \times 12}{15+12} = 6.67 \Omega$$

$$I_{15} = \frac{12}{12+15} \times 3.6$$

$$I = \frac{V}{R_{eq}} = \frac{24}{6.67}$$

$$= 3.59$$


$$= 3.6 \text{ A}$$

2018

4.C) A 10mV, 5 KHz sinusoidal signal is applied to the input of an OP-AMP integration as shown below for which $R = 100\text{ k}\Omega$ & $C = 1 \mu\text{F}$. Find output voltage.

Solⁿ:

We know,

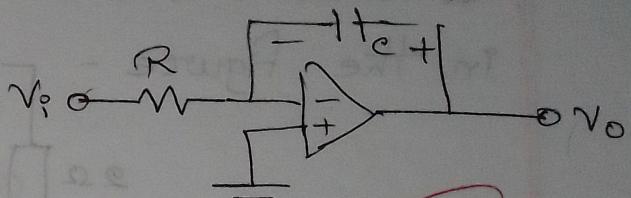

$$V_{\text{out}} = -\frac{1}{RC} \int v_i(t) dt$$

$$= -\frac{1}{RC} \int v_0 \sin \omega t dt$$

$$= -\frac{v_0}{RC} \left(-\frac{\cos \omega t}{\omega} \right) + C$$

$$= \frac{v_0 \cos \omega t}{RC \omega}$$

$$= \frac{10 \times 10^{-3} \times \cos(2\pi \times 5000 \times 5 \times 10^3 t)}{100 \times 10^3 \times 1 \times 10^{-6} \times 2\pi \times 5 \times 10^3}$$

$$= 3.16 \times 10^{-6} \cos(31416t) \quad (\text{Ans})$$

$$(51 + 12j)^{-1}$$

$$= \frac{1}{51 + 12j}$$